



Ballparking SOC parameters

- If the model uses a single parallel R–C branch, it's quite simple to get a ballpark idea of model's parameter values
 - We will improve on these methods later in the course

$$z[k+1] = z[k] - \frac{\eta[k]\Delta t}{Q}i[k]$$

$$i_{R_1}[k+1] = \exp\left(-\frac{\Delta t}{R_1C_1}\right)i_{R_1}[k] + \left(1 - \exp\left(-\frac{\Delta t}{R_1C_1}\right)\right)i[k]$$

$$v[k] = \text{OCV}(z[k]) - R_1i_{R_1}[k] - R_0i[k]$$

- Can compute Q by discharging cell slowly from 100 % to 0 % SOC and recording ampere hours removed
- Can find η by charging from 0 % to 100 % SOC, computing discharge capacity divided by charge capacity
- Can average dis/charge voltages at every SOC to find $\text{OCV}(z[k])$




Ballparking R_0 parameter

- Next, conduct pulse test; notice instantaneous voltage change

$$z[k+1] = z[k] - \frac{\eta[k]\Delta t}{Q}i[k]$$

$$i_{R_1}[k+1] = \exp\left(-\frac{\Delta t}{R_1C_1}\right)i_{R_1}[k] + \left(1 - \exp\left(-\frac{\Delta t}{R_1C_1}\right)\right)i[k]$$
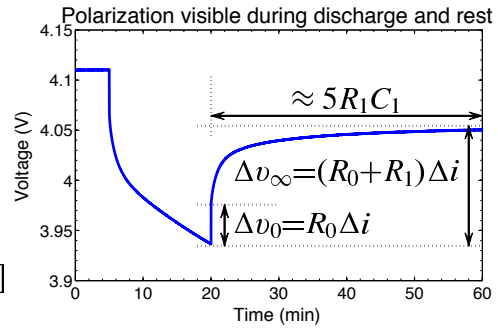
$$v[k] = \text{OCV}(z[k]) - R_1i_{R_1}[k] - R_0i[k]$$



- Only $-R_0i[k]$ changes instantly, so response to removal of pulse $|\Delta v_0| = R_0|\Delta i|$




Ballparking R_1 parameter

- Next, consider steady-state voltage change after pulse

$$z[k+1] = z[k] - \frac{\eta[k]\Delta t}{Q}i[k]$$

$$i_{R_1}[k+1] = \exp\left(-\frac{\Delta t}{R_1C_1}\right)i_{R_1}[k] + \left(1 - \exp\left(-\frac{\Delta t}{R_1C_1}\right)\right)i[k]$$
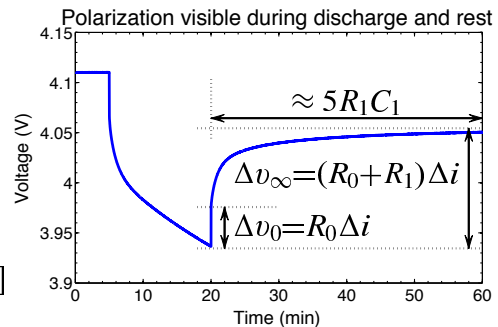
$$v[k] = \text{OCV}(z[k]) - R_1i_{R_1}[k] - R_0i[k]$$



- $|\Delta v_\infty| = (R_0 + R_1)|\Delta i|$, from which we can deduce R_1




Ballparking C_1 parameter

- Finally, consider time to decay to steady-state

$$z[k+1] = z[k] - \frac{\eta[k]\Delta t}{Q} i[k]$$

$$i_{R_1}[k+1] = \exp\left(-\frac{\Delta t}{R_1 C_1}\right) i_{R_1}[k] + \left(1 - \exp\left(-\frac{\Delta t}{R_1 C_1}\right)\right) i[k]$$
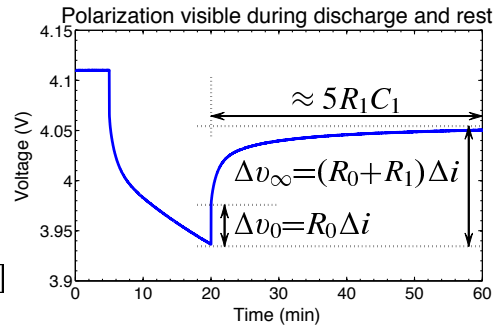
$$v[k] = \text{OCV}(z[k]) - R_1 i_{R_1}[k] - R_0 i[k]$$



- Pulse response converges to steady state in about five time constants, $\Delta t = 5R_1C_1$, from which we can deduce C_1




Example with values

- For cell test conducted to gather plotted data, $|\Delta i| = 5 \text{ A}$, $|\Delta v_0| = 41 \text{ mV}$, and $|\Delta v_\infty| = 120 \text{ mV}$
- We then compute $R_0 \approx 8.2 \text{ m}\Omega$ and $R_1 \approx 15.8 \text{ m}\Omega$
- Time to steady-state is about $60 \text{ min} - 20 \text{ min} = 40 \text{ min} = 2400 \text{ s}$
- So,

$$5R_1C_1 \approx 2400 \text{ s} \quad \text{and} \quad C_1 \approx 480/R_1$$

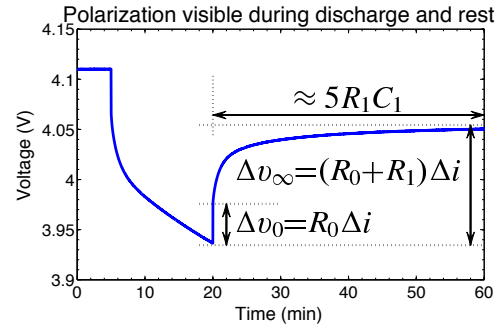- Using R_1 from above, $C_1 \approx 30 \text{ kF}$



Summary

- Have seen simple procedure to approximate parameter values for model having a single R-C branch
- Simple dis/charge test used to determine values for Q , η , OCV
- Pulse discharge finds R_0 , R_1 , C_1
- If model uses multiple parallel R-C branches in series, this simple approach will not work—we'll look at another approach later

