## Summary of this week



- We have now fully derived ESC cell model: describes SOCdependent OCV, ohmic and diffusion voltages, hysteresis
- ESC "state equation" describes all dynamic effects (cf. slide 4 re.  $A_{RC}$ ,  $B_{RC}$ ,  $A_H$ )

$$\underbrace{\begin{bmatrix} z[k+1] \\ i_R[k+1] \\ h[k+1] \end{bmatrix}}_{x[k+1]} = \underbrace{\begin{bmatrix} 1 & 0 & 0 \\ 0 & A_{RC} & 0 \\ 0 & 0 & A_H[k] \end{bmatrix}}_{A[k]} \underbrace{\begin{bmatrix} z[k] \\ i_R[k] \\ h[k] \end{bmatrix}}_{x[k]} + \underbrace{\begin{bmatrix} -\eta[k]\Delta t/Q & 0 \\ B_{RC} & 0 \\ 0 & A_H[k] - 1 \end{bmatrix}}_{B[k]} \underbrace{\begin{bmatrix} i[k] \\ \text{sgn}(i[k]) \end{bmatrix}}_{u[k]}$$

■ ESC "output equation" computes voltage

$$v[k] = OCV(z[k], T[k]) + M_0s[k] + Mh[k] - \sum_i R_i i_{R_i}[k] - R_0i[k]$$

Dr. Gregory L. Plett University of Colorado Colorado Springs

Equivalent Circuit Cell Model Simulation | Defining an ECM of a Li-ion cell 1 of 4

2.1.9: Where from here?


## Summary of this week (continued)



- Model be visualized as an equivalent circuit
- Mathematically it comprises two coupled equations

$$x[k+1] = A[k]x[k] + B[k]u[k]$$
$$v[k] = f(x[k], u[k])$$

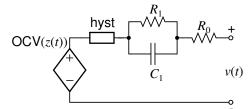■ This "state-space" model structure will be vitally important in Course 3 of the specialization, on SOC estimation



Dr. Gregory L. Plett University of Colorado Colorado Springs

Equivalent Circuit Cell Model Simulation | Defining an ECM of a Li-ion cell

2.1.9: Where from here?

## Where from here?



- We now begin to consider how to find the parameter values of the model equations
- You will learn how to find the static parts of the relationship
  - What kinds of lab equipment are needed to characterize a particular cell?
  - What laboratory tests do we perform?
  - □ How do we compute coulombic efficiency?
  - □ How do we determine cell OCV?
- You will also see Octave/MATLAB code to perform these computations



## **Credits**



Credits for photo in this lesson

■ "What's next?" on slide 2: By Sarah Reid, [CC BY 2.0

(https://creativecommons.org/licenses/by/2.0/)], https://www.flickr.com/photos/sarahreido/4683295771

In the earlier slides, note that

$$A_{RC} = \begin{bmatrix} \exp\left(\frac{-\Delta t}{R_1 C_1}\right) & 0 & \cdots \\ 0 & \exp\left(\frac{-\Delta t}{R_2 C_2}\right) \\ \vdots & \ddots \end{bmatrix}, \qquad B_{RC} = \begin{bmatrix} \left(1 - \exp\left(\frac{-\Delta t}{R_1 C_1}\right)\right) \\ \left(1 - \exp\left(\frac{-\Delta t}{R_2 C_2}\right)\right) \\ \vdots & \vdots \end{bmatrix}$$
$$A_H[k] = \exp\left(-\left|\frac{\eta[k]i[k]\gamma \Delta t}{Q}\right|\right)$$

Dr. Gregory L. Plett University of Colorado Colorado Springs

Equivalent Circuit Cell Model Simulation | Defining an ECM of a Li-ion cell 4 of 4